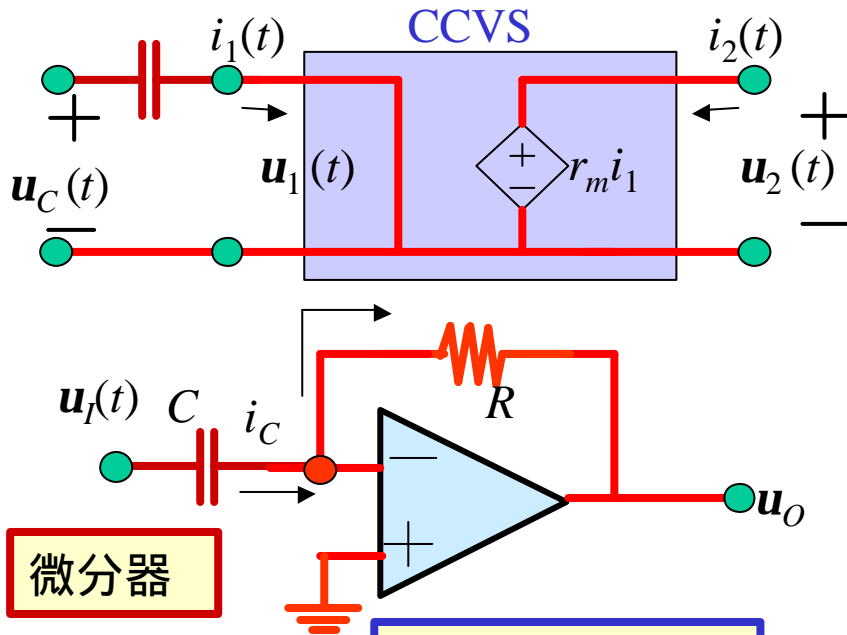


主動式積分器、微分器與濾波器

主動式積分器、微分器




微分器

$$i_C = C \frac{du_I(t)}{dt}$$

$$u_O(t) = -CR \frac{du_I(t)}{dt}$$

$$\frac{V_o}{V_i} = -sCR$$
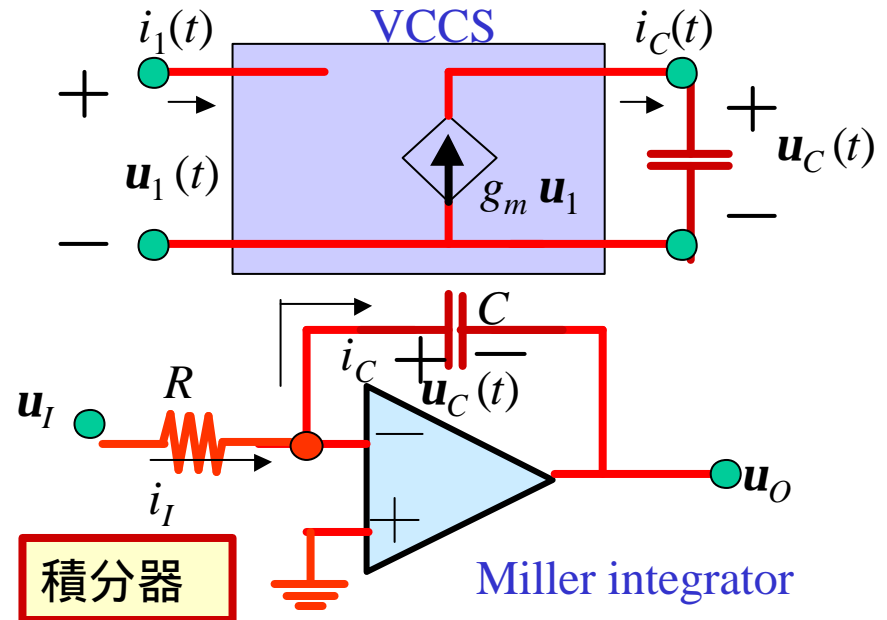
$$i = C \frac{du}{dt} \quad u = \frac{1}{C} \int_{t_0}^t i dt + u(t_0)$$




積分器

Miller integrator

$$u_O(t) = -\frac{1}{CR} \int_0^t u_I(t) dt + u_O(0)$$

$$\frac{V_o}{V_i} = -\frac{1}{sCR}$$

有關Miller integrator

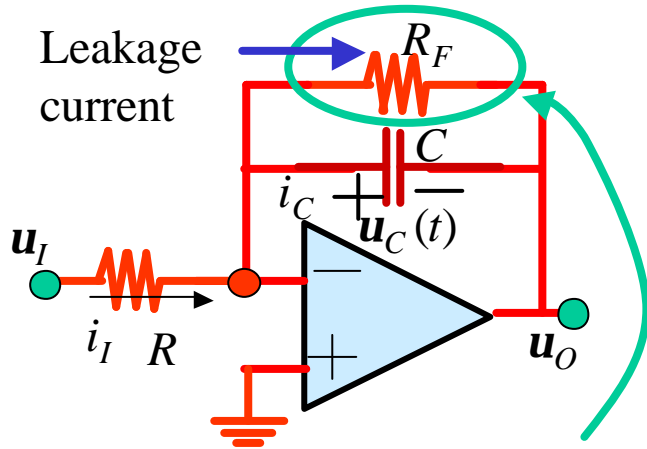

通常會加一個大電阻提供DC的回授


例題

$$R=10\text{k}\Omega, C=10\text{nF}, R_F=1\text{M}\Omega$$


$$R_F C=10\text{ms}$$

$$\text{Charging current } i_I=1\text{V}/10\text{k}\Omega=0.1\text{mA}$$

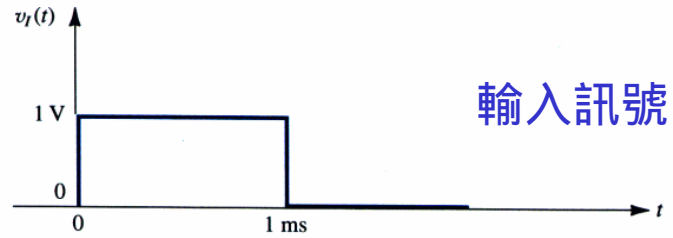
$$i_I R_F=0.1\text{mA} \cdot 1\text{M}\Omega=100\text{V}$$



(a)

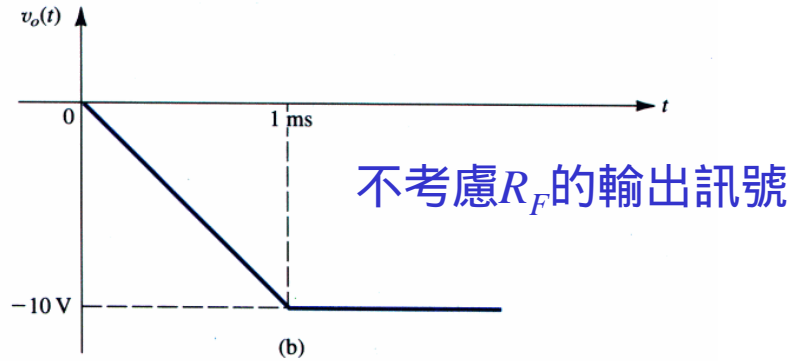


(b)

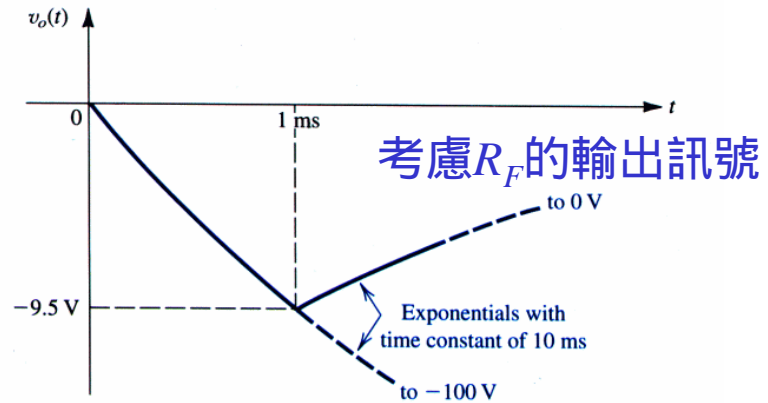

(c)


主動式濾波器

簡易主動式濾波器

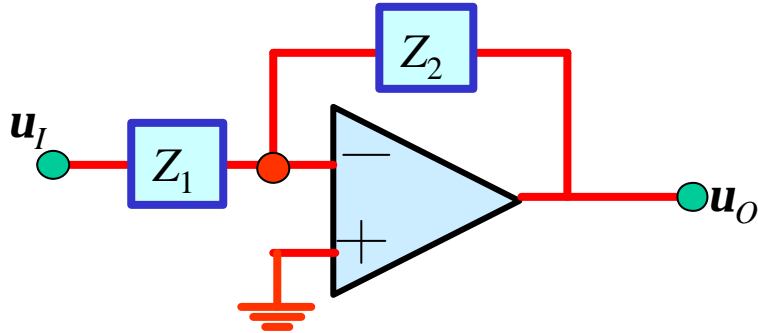


$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

Inverting configuration

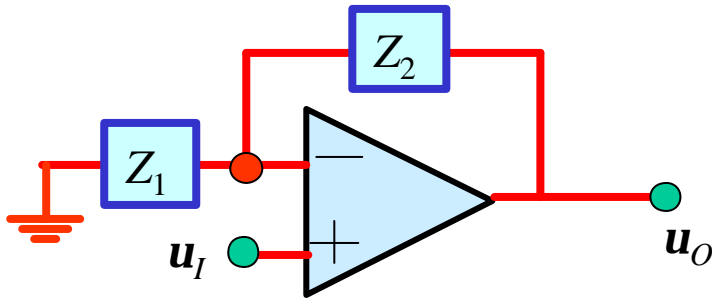


$$\frac{V_o(s)}{V_i(s)} = 1 + \frac{Z_2(s)}{Z_1(s)}$$

Noninverting configuration

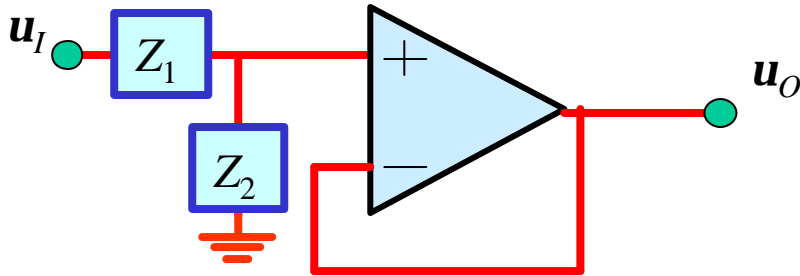

$$\frac{V_o(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

例題

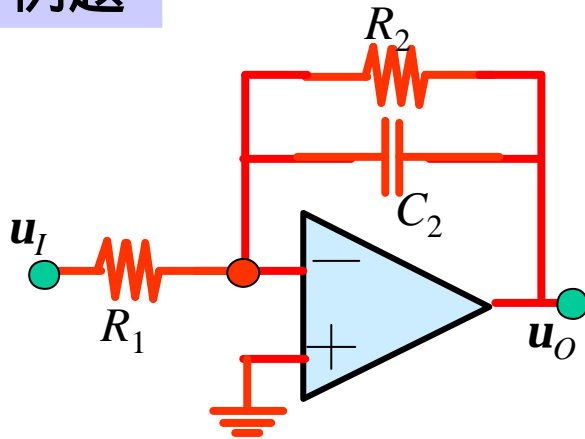

$$\begin{aligned}\frac{V_o(s)}{V_i(s)} &= -\frac{Z_2(s)}{Z_1(s)} = -\frac{R_2 + \frac{1}{sC_2}}{R_1} \\ &= -\frac{1}{R_1} \frac{R_2 \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = -\frac{R_2}{R_1} \left(\frac{1}{1 + sR_2C_2} \right)\end{aligned}$$


A_0

$$T(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = A_0 \left(\frac{1}{1 + j\omega R_2 C_2} \right) = A_0 \left(\frac{1}{1 + j\omega / \omega_H} \right)$$


$$\omega_H = 1 / R_2 C_2$$

為一個有增益的低通濾波器

波德圖如下

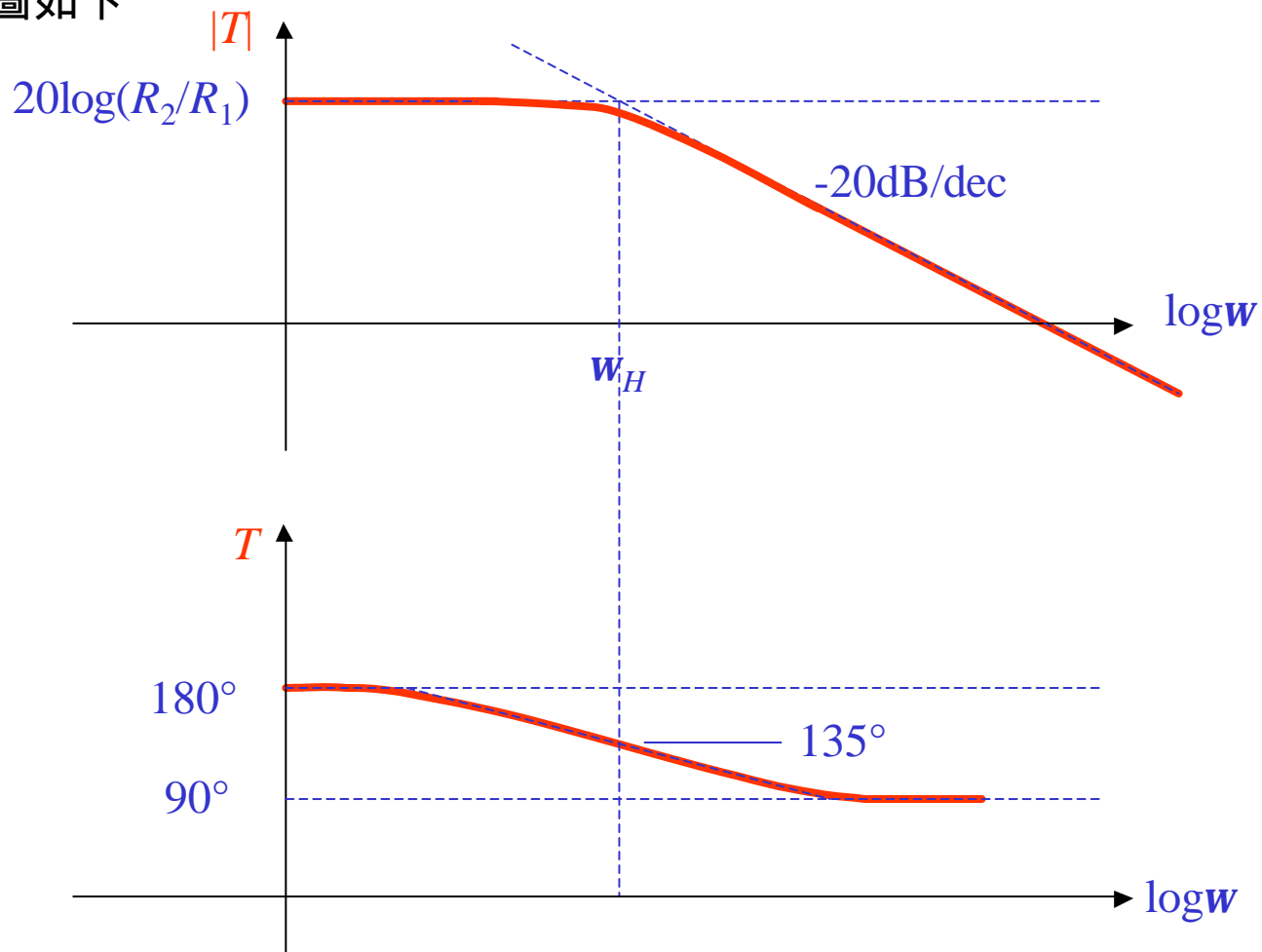

例題

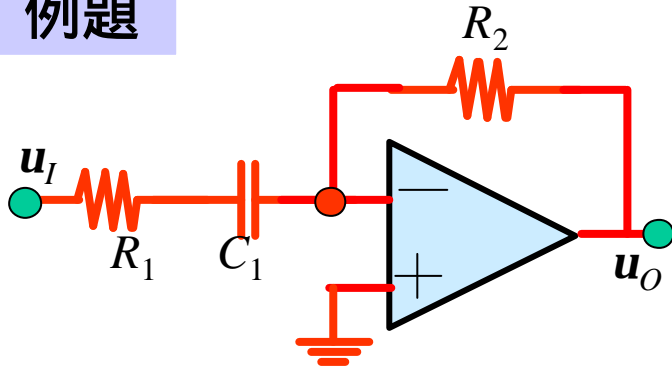

$$\begin{aligned}\frac{V_o(s)}{V_i(s)} &= -\frac{Z_2(s)}{Z_1(s)} = -\frac{R_2}{R_1 // \frac{1}{sC_1}} \\ &= -\frac{R_2 s C_1}{1 + s R_1 C_1} = \underline{-\frac{R_2}{R_1} \left(\frac{s R_1 C_1}{1 + s R_1 C_1} \right)}\end{aligned}$$

A

$$T(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = A_\infty \left(\frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \right) = A_\infty \left(\frac{j\omega / \omega_L}{1 + j\omega / \omega_L} \right)$$

$$\omega_L = 1 / R_1 C_1$$

為一個有增益的高通濾波器

波德圖自行練習畫

討論

主動式與被動式濾波器各有何優缺點？