

# 運算放大器的頻率響應

典型的運算放大器增益的頻率響應---很大的DC gain , 很低的頻寬


簡易模型—STC circuit

$$A(j\omega) = \frac{A_0}{1 + j\omega / \omega_b}$$

當  $\omega \gg \omega_b$

$$A(j\omega) \approx \frac{A_0}{j\omega / \omega_b} = j \frac{\omega_b A_0}{\omega}$$


$$|A(j\omega_t)| = \frac{\omega_b A_0}{\omega_t} = 1 \Rightarrow \omega_t = \omega_b A_0$$

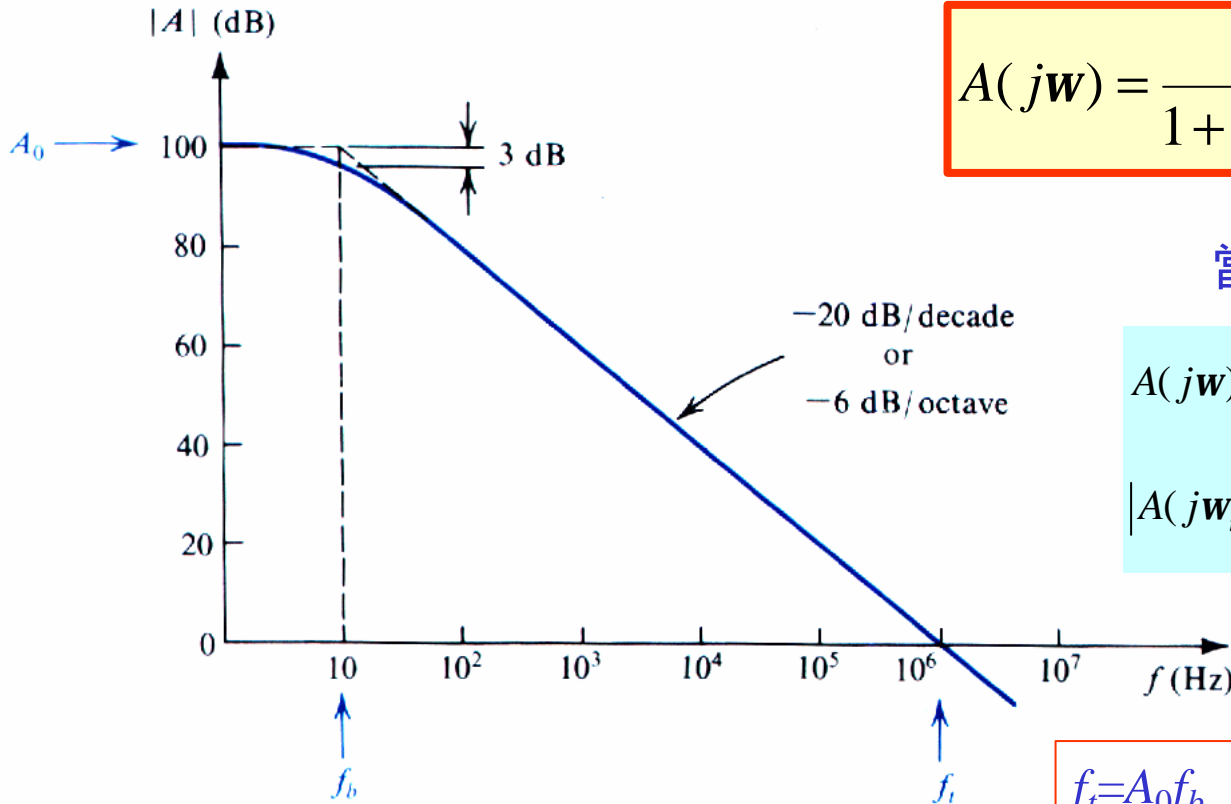

$$f_t = A_0 f_b$$

Unity-gain freq.

# 對close-loop gain的影響

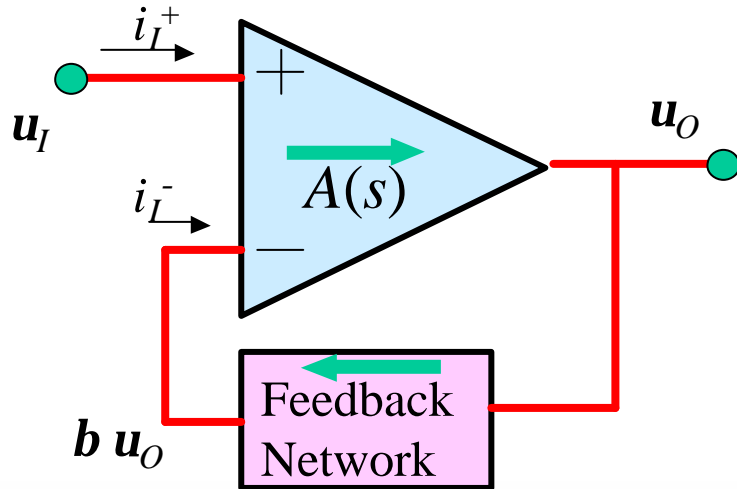

$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{A(s)}{1 + bA(s)}$$


$$A(j\omega) \approx \frac{A_0}{j\omega / \omega_b} = j \frac{\omega_b A_0}{\omega}$$

$$|A(j\omega_{3dB})| = \frac{\omega_b A_0}{\omega_{3dB}} = \frac{1}{b} \Rightarrow \omega_{3dB} = b\omega_b A_0$$


$$\frac{\omega_{3dB}}{b} = \omega_b A_0 = \omega_{3dB} G_0$$

$$\omega_b A_0 = \omega_{3dB} G_0 = \omega_t \cdot 1$$


Gain-bandwidth product

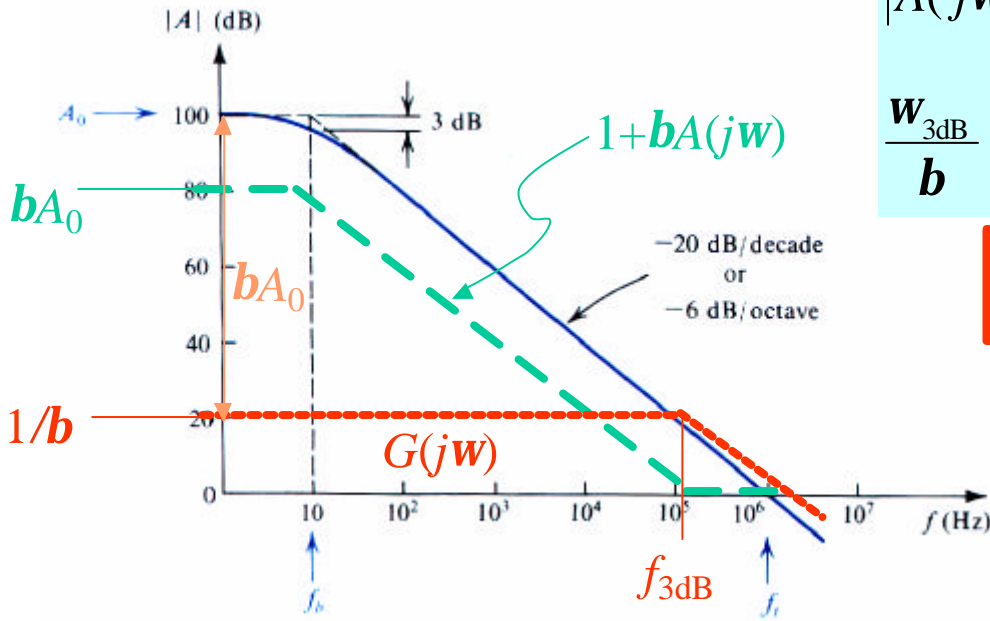

# 例題

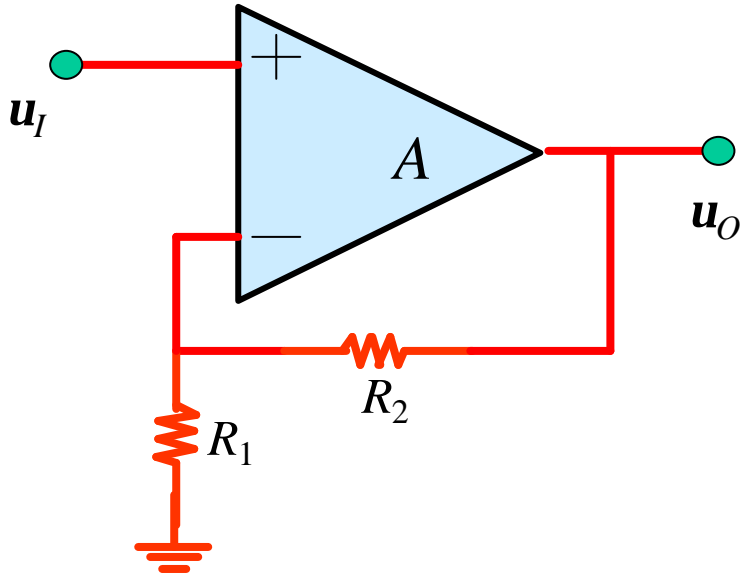
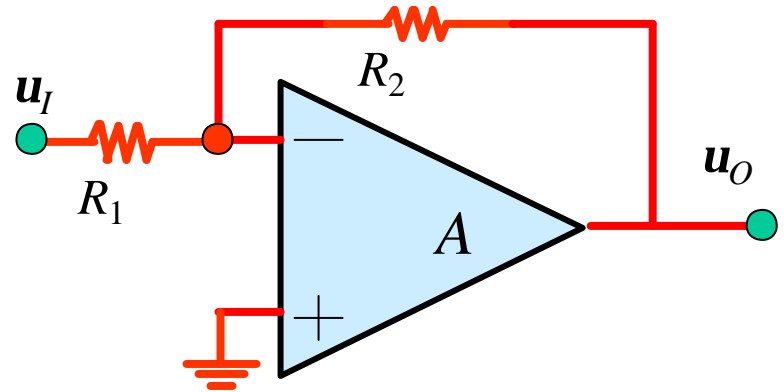
$$\begin{aligned}
 G &= \frac{V_o(s)}{V_i(s)} = \frac{1}{R_1/(R_1 + R_2) + 1/A(s)} \\
 &= \frac{1}{\frac{R_1}{R_1 + R_2} + \frac{1}{A_0} + \frac{s}{A_0 w_b}} \\
 &= \frac{1 + R_2/R_1}{1 + \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right) + \frac{s}{w_t/(1 + R_2/R_1)}}
 \end{aligned}$$



$$\begin{aligned}
 G &= \frac{V_o(s)}{V_i(s)} = -\frac{R_2/R_1}{1 + (1 + R_2/R_1)/A(s)} \\
 &= -\frac{R_2/R_1}{1 + \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right) + \frac{s}{w_t/(1 + R_2/R_1)}}
 \end{aligned}$$

## 例題

Consider an op amp with  $f_t = 1\text{ MHz}$ . Find the 3-dB frequency of closed-loop amplifiers with nominal gains of +1000, +100, +10, +1, -1, -10, -100, -1000. Sketch the magnitude frequency response for the amplifiers with closed-loop gains of +10 and -10.

Closed-Loop Gain	$\frac{R_2}{R_1}$	$f_{3\text{dB}} = f_t / (1 + R_2/R_1)$
+1000	999	1 kHz
+100	99	10 kHz
+10	9	100 kHz
+1	0	1 MHz
-1	1	0.5 MHz
-10	10	90.9 kHz
-100	100	9.9 kHz
-1000	1000	$\approx 1\text{ kHz}$

