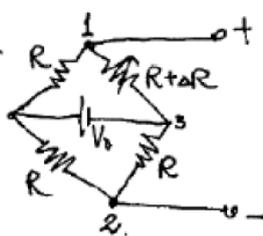


作業一解答

1-5 略

6.



先求 open-circuit voltage V_{oc}

$$V_{13} = V_1 - V_3 = \frac{R+\Delta R}{R+R+\Delta R} V_0 = \frac{R+\Delta R}{2R+\Delta R} V_0$$

$$V_{23} = V_2 - V_3 = \frac{R}{R+R} V_0 = \frac{1}{2} V_0$$

$$V_{oc} = V_{12} = V_{13} - V_{23}$$

$$= V_0 \left[\frac{1 + \frac{\Delta R}{R}}{2 + \frac{\Delta R}{R}} - \frac{1}{2} \right]$$

$$\approx \frac{1}{2} \left(1 + \frac{\Delta R}{R} \right) \left(1 + \frac{\Delta R}{2R} \right)^{-1}$$

$$\approx \frac{1}{2} \left(1 + \frac{\Delta R}{R} \right) \left[1 - \frac{\Delta R}{2R} + O\left(\frac{\Delta R^2}{R^2}\right) \right]$$

$$\approx \frac{1}{2} + \frac{\Delta R}{2R} - \frac{\Delta R}{4R} + O\left(\frac{\Delta R^2}{R^2}\right)$$

$$\approx \frac{1}{2} + \frac{\Delta R}{4R} \quad \text{因 } \frac{\Delta R}{R} \ll 1$$

$$V_{oc} = \frac{\Delta R}{4R} V_0$$

再求輸出電阻 R_{th} , 將 V_0 拿掉 (短路!)

$$R_{th} = R//R + R//(R+\Delta R)$$

$$= \frac{1}{2}R + \frac{R(R+\Delta R)}{R+R+\Delta R} = R + \frac{\Delta R}{4} \approx R$$




$$= \frac{R+\Delta R}{2 + \frac{\Delta R}{R}}$$


$$= \frac{R}{2} \left(1 + \frac{\Delta R}{R} \right) \left(1 + \frac{\Delta R}{2R} \right)^{-1} = \frac{R}{2} \left(1 + \frac{\Delta R}{R} \right) \left[1 - \frac{\Delta R}{2R} + O\left(\frac{\Delta R^2}{R^2}\right) \right]$$

$$\approx \frac{R}{2} \left[1 + \frac{\Delta R}{2R} \right] = \frac{R}{2} + \frac{\Delta R}{4}$$

戴維寧等值電路為

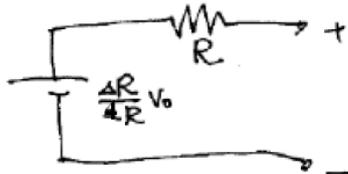

7.(1)

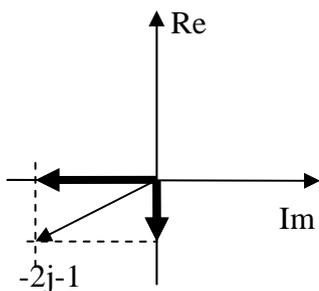

(2)

