

Solutions for Homework #6

1.

4.1

Case	mode
1	active
2	saturation
3	active
4	saturation
5	inverted active mode
6	active
7	cut-off
8	cut-off

2.

4.7

$$i_c = \beta i_b$$

$$400 = \beta \cdot 7.5$$

$$\beta = \frac{400}{7.5} = \underline{\underline{53.3}}$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{53.3}{54.3} = \underline{\underline{0.982}}$$

3

4.9

$$i_c = I_s e^{v_{BE}/V_T}$$

$$i_b = \frac{i_c}{\beta}$$

$$i_E = \frac{\beta + 1}{\beta} i_c$$

$$i_c = (5 \times 10^{-15}) e^{0.650/0.025} = 977 \mu\text{A}$$

i_c is constant and independent of β

$$i_b \text{ ranges from } \frac{i_c}{\beta} = \frac{977 \times 10^{-6}}{50} = 19.6 \mu\text{A}$$

$$\text{to } \frac{i_c}{\beta} = \frac{977 \times 10^{-6}}{200} = 4.89 \mu\text{A}$$

i_E ranges from

$$\frac{\beta + 1}{\beta} i_c = \frac{51}{50} 977 \times 10^{-6} = 998 \mu\text{A}$$

$$\text{to } \frac{\beta + 1}{\beta} i_c = \frac{201}{200} 977 \times 10^{-6} = 983 \mu\text{A}$$

4.

4.10

$$i_E = 1 \text{ mA}$$

$$\text{Case I: } i_B = 50 \mu\text{A}$$

$$i_C = i_E - i_B = 1 \times 10^{-3} - 50 \times 10^{-6} = 950 \mu\text{A}$$

$$\beta = \frac{i_C}{i_B} = \frac{950 \times 10^{-6}}{50 \times 10^{-6}} = 19$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{19}{20} = 0.95$$

$$\text{Case II: } i_B = 10 \mu\text{A}$$

$$i_C = i_E - i_B = 1 \times 10^{-3} - 10 \times 10^{-6} \text{ A}$$

$$= 990 \mu\text{A}$$

$$\beta = \frac{i_C}{i_B} = \frac{990 \times 10^{-6}}{10 \times 10^{-6}} = 99$$


$$\alpha = \frac{\beta}{\beta + 1} = \frac{99}{100} = 0.99$$

5


4.19

(a) $I_1 = \frac{10.7 - 0.7}{10} = 1 \text{ mA}$


(b)

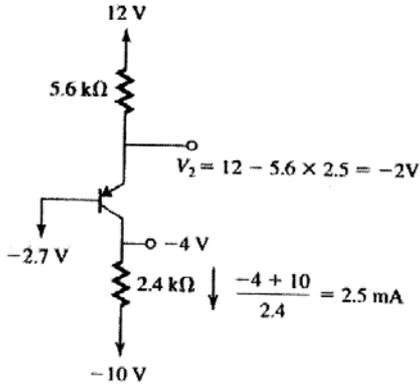

(c)

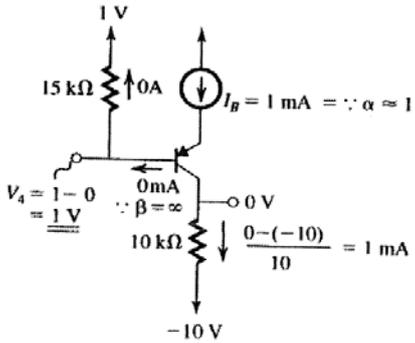

(d)

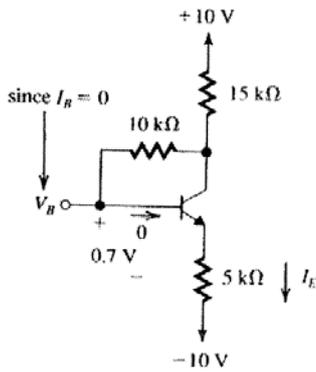

$I_E = I_C$

$\frac{V_B - 0.7 + 10}{5} = \frac{10 - V_E}{15}$

$15V_6 + 139.5 = 50 - 5V_6$


$V_6 = -4.475 \text{ V}$

$I_3 = \frac{V_6 - 0.7 + 10}{5}$


$= \frac{-4.475 - 0.7 + 10}{5} = 0.965 \text{ mA}$

6.

4.20

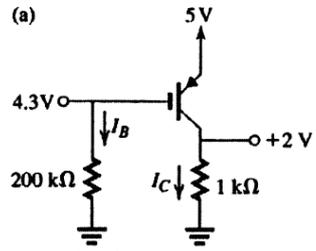

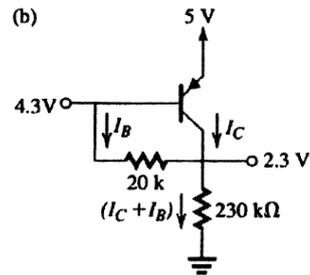
$\frac{I_C}{I_B} = \beta = \frac{\left(\frac{2}{1 \text{ K}}\right)}{\left(\frac{4.3}{200 \text{ K}}\right)} = \frac{2 \text{ m}}{0.0215 \text{ m}} = 93$



$(I_C + I_B) = \frac{2.3}{230} = 10 \text{ mA}$

$I_B = \left(\frac{4.3 - 2.3}{20 \text{ K}}\right) = 0.1 \text{ mA}$

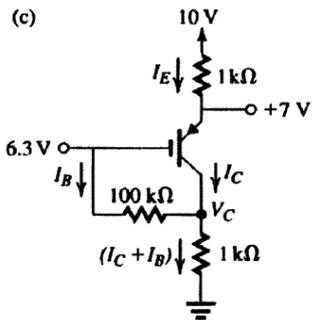$\frac{I_C}{I_B} = \left(\frac{10 \text{ m} - 0.1 \text{ m}}{0.1 \text{ m}}\right) = \beta = 99$



$I_E = \left(\frac{10 - 7}{1 \text{ K}}\right) = 3 \text{ mA}$

$I_E = I_C + I_B = 3 \text{ mA}$

$V_C = 3 \text{ m}(1 \text{ K}) = 3 \text{ V}$

$I_B = \frac{6.3 - 3}{100 \text{ K}} = 33 \text{ } \mu\text{A}$

$\frac{I_E}{I_B} = \beta + 1 = \frac{3 \text{ m}}{33 \text{ } \mu} = 90.9$

$\beta = 89.9$

7.&8.略